

Aperivox


Designed June 2014 by John Hollander




The purpose of the project was to remake a pair of home theater main speakers. The mid-range was planned to be open back in a narrow baffle. This necessitated the MTW arrangement and the tapered top portion of the baffle. The drivers are the RS225S-8, RS150S-8, and the RS28A-4. The tweeter is still available.

The woofer section is designed and damped as a MLTL. The box volume is about 49 liters, with an f3 in the mid 30s


The crossover points were dictated by the dipole null and roll off of the midrange. The tweeter to mid crossover is at 1,900 Hz, 3rd order Butterworth shape. The mid to woofer is about 700 Hz, second order Bessel shape

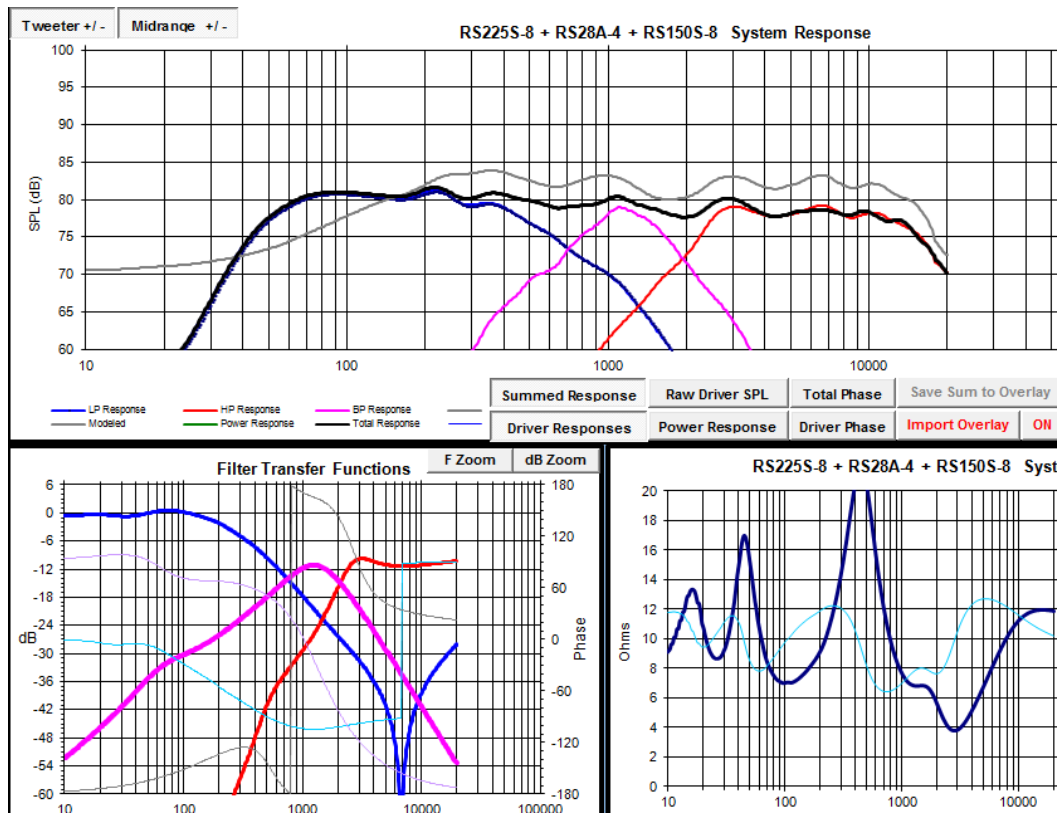This graph is measured over modeled. Note that the simulation is tilted down toward the high frequencies, but the measured response is flat. This is due to the open baffle rear wave. Driver responses are not accurate below 80Hz due to the test enclosure. Actual measurement was gated at 350 Hz



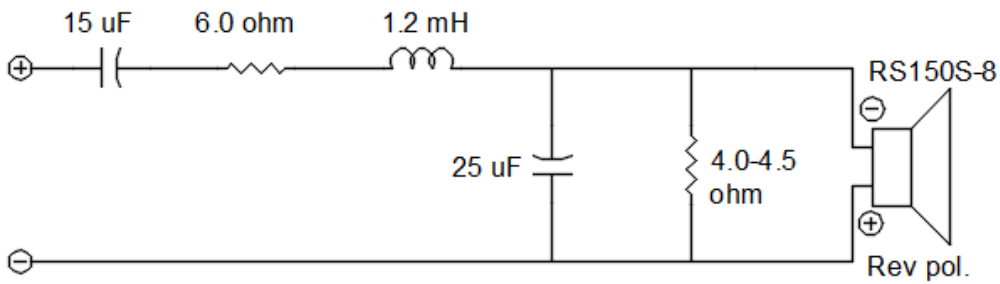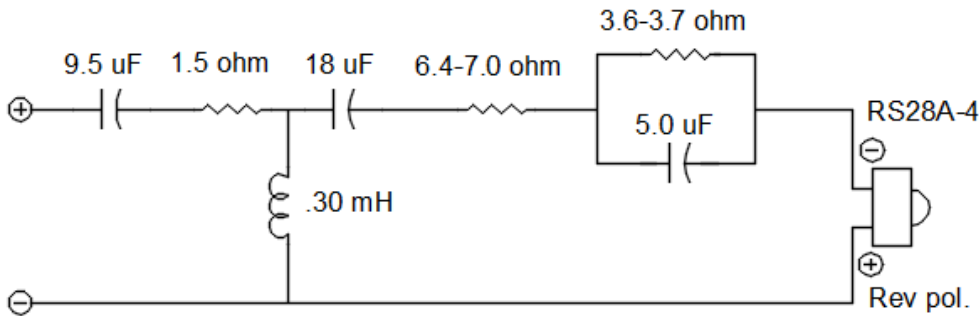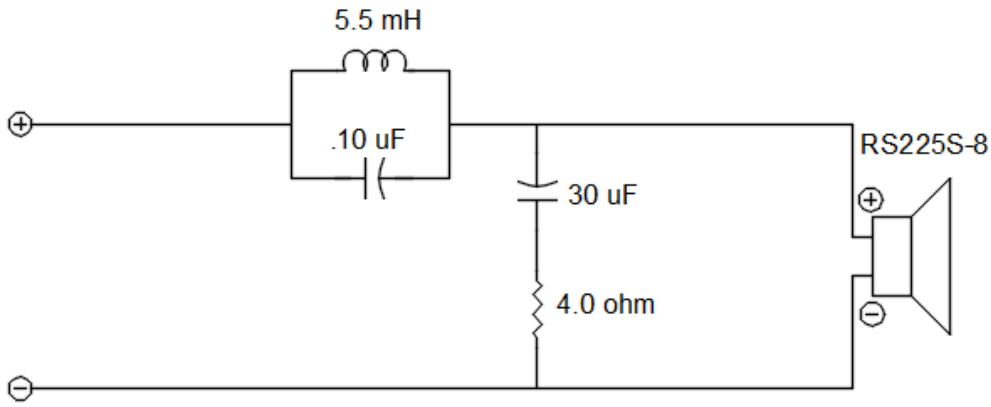


Woofer Low Pass Crossover Design Section			
Target Transfer Function	Import Target Response		
Select Desired Response Shape	Enter	Enter	
Target Transfer Function	Frequency	Level	
Second Order Bessel Target	550 Hz	80.0	
Woofer Low Pass Circuit Selections and Component Values			
Select Low Pass Crossover Order	Crossover Component Values in mH, uF, & Ohms		DCR or Series R
Selected Filter:	L 2 mH	C 0.00	0.50
First Order Parallel			
Selected Electrical Frequency:	800 Hz		
Initialize Textbook Values	Clear Crossover Values		
Select Topology to be in Series Before or After LP Filter	Enter Appropriate Values for Circuit		
Before Crossover - Selected Circuit:	L mH	C uF	R Ohm
Parallel RLC Notch Filter	5.50	0.10	#####
After Crossover - Selected Circuit:	No Series Elements		
Select Topology to be in Parallel With Woofer	Enter Appropriate Values for Circuit		
Parallel Leg 1 - Selected Circuit:	L mH	C uF	R Ohm
Series RC (Zobel)	30.00	4.00	

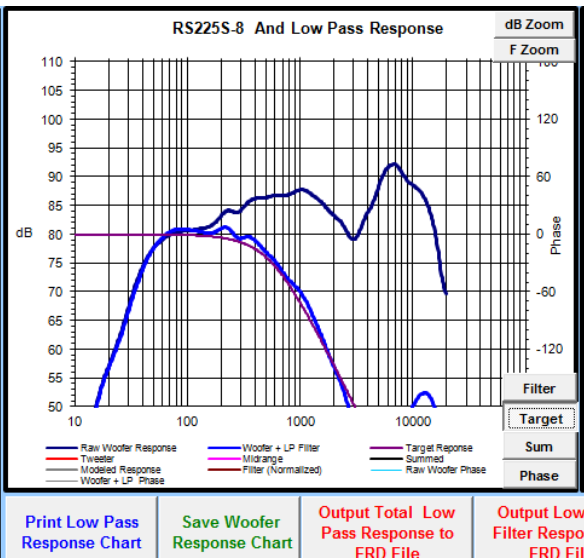


Tweeter High Pass Crossover Design Section

Target Transfer Function		Import Target Response	
Select Desired Response Shape		Enter	Enter dB
Target Transfer Function	Frequency	Level	
Third Order Butterworth Target	1,500 Hz	79.0	
Tweeter High Pass Circuit Selections and Component Values			
Select High Pass Crossover Order		Crossover Component Values in mH, uF, & Ohms	
Selected Filter Order:	C9 uF	9.50	1.50
Third Order Parallel	L9 mH	0.30	0.34
Selected Electrical Frequency:	C10 uF	18.00	6.50
1,500 Hz			
Initialize Textbook Values		Clear Crossover Values	
Select Topology to be in Series Before or After HP Filter		Enter Appropriate Values for Circuit	
	L mH	C uF	R Ohm
Before Crossover - Selected Circuit:	No Series Elements		
After Crossover - Selected Circuit:	5.00 3.70		
Parallel RC Contour Filter			
Select Topology to be in Parallel		Enter Appropriate Values for Circuit	


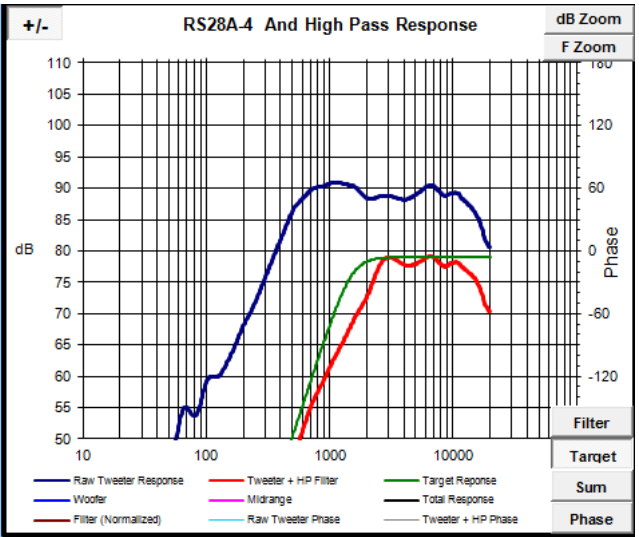



Midrange Band Pass Crossover Design Section

High Pass Target Transfer Function		Import BP Target Response	
Select Desired Response Shape		Enter	Enter dB
Target Transfer Function	Frequency	Level	
Second Order Bessel Target	550 Hz	80.0	
Low Pass Target (Use High Pass Above For Selecting Imported Target)			
Select Desired Response Shape		Enter	Enter dB
Target Transfer Function	Frequency	Level	
Third Order Butterworth Target	1,500 Hz	80.0	
High Pass Circuit Selections and Component Values			
Select Midrange High Pass Crossover Order		Crossover Component Values in mH, uF, & Ohms	
Selected Filter Order:	C16 uF	15.00	6.00
First Order Electrical			
Selected Electrical Frequency:	800 Hz		
Initialize Textbook Values		Clear Crossover Values	
Low Pass Circuit Selections and Component Values			
Select Midrange Low Pass Crossover Order		Crossover Component Values in mH, uF, & Ohms	
Selected Filter:	L18 mH	1.20	0.77
Second Order Electrical	C18 uF	25.00	
Selected Electrical Frequency:	1,500 Hz		
Initialize Textbook Values		Clear Crossover Values	
Select Topology to be in Series Before or After Crossover Filter		Enter Appropriate Values for Circuit	
	L mH	C uF	R Ohm
Before Crossover - Selected Circuit:	No Series Elements		
After Crossover - Selected Circuit:	No Series Elements		
Select Topology to be in Parallel With Midrange		Enter Appropriate Values for Circuit	
	L mH	C uF	R Ohm
Parallel Leg 1 - Selected Circuit:	4.25		
Parallel Resistor			

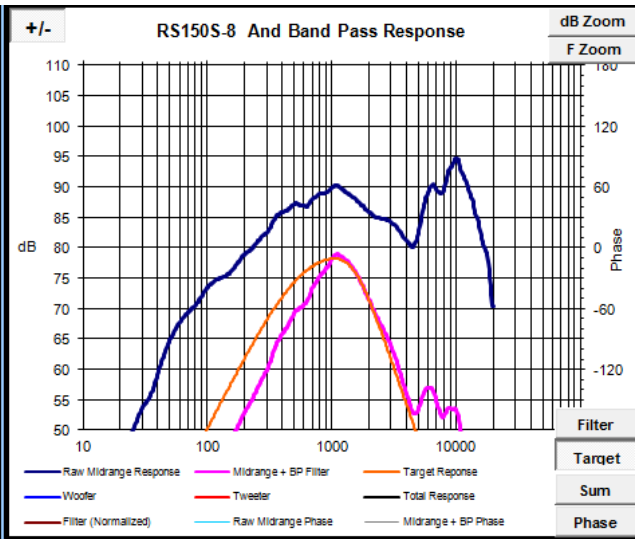

Print Band Pass Response Chart	Save Midrange Response Chart	Output Summed Midrange Response to FRD File	Output Band Filter Response to FRD File
View PCD Circuit Layouts	Two-Way Crossover Calculators	Three-Way Crossover Calculators	

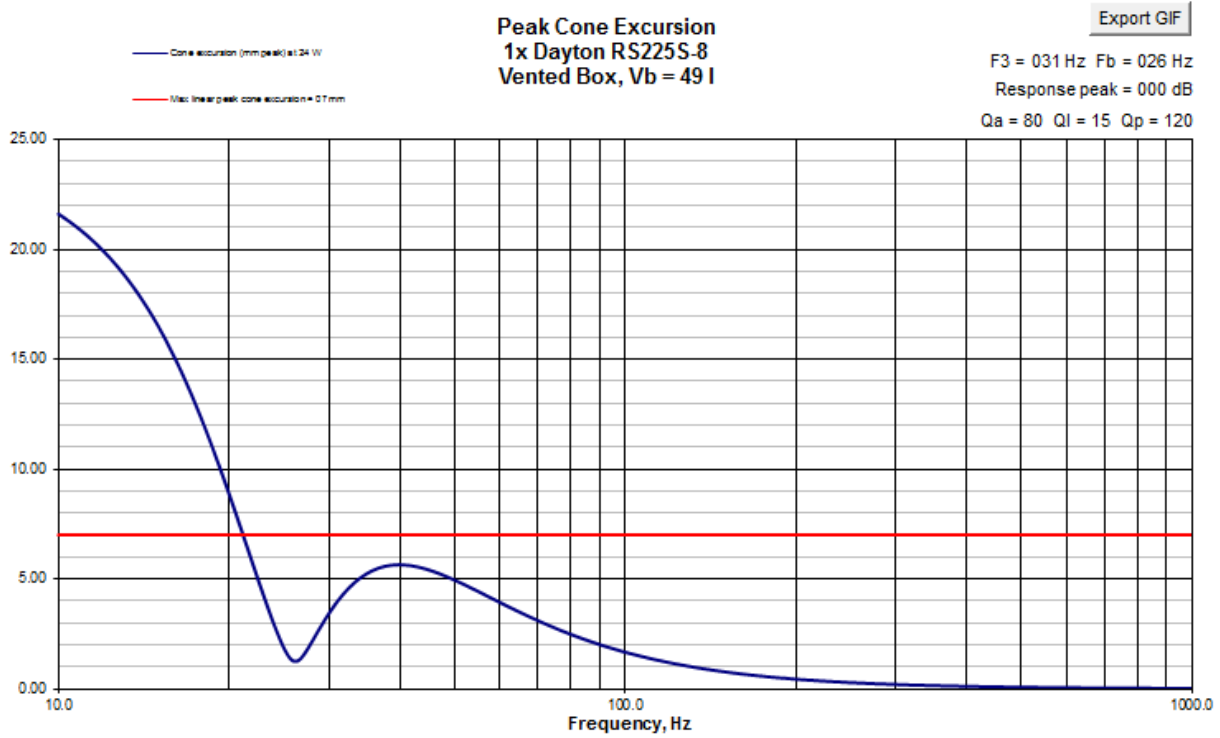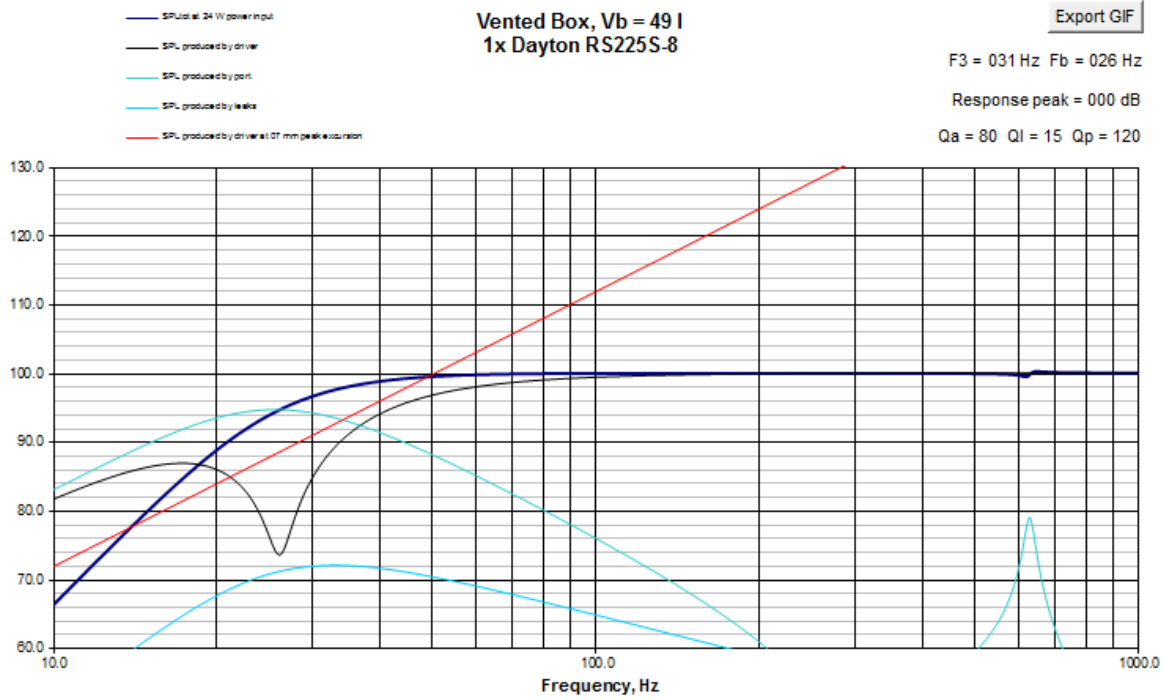

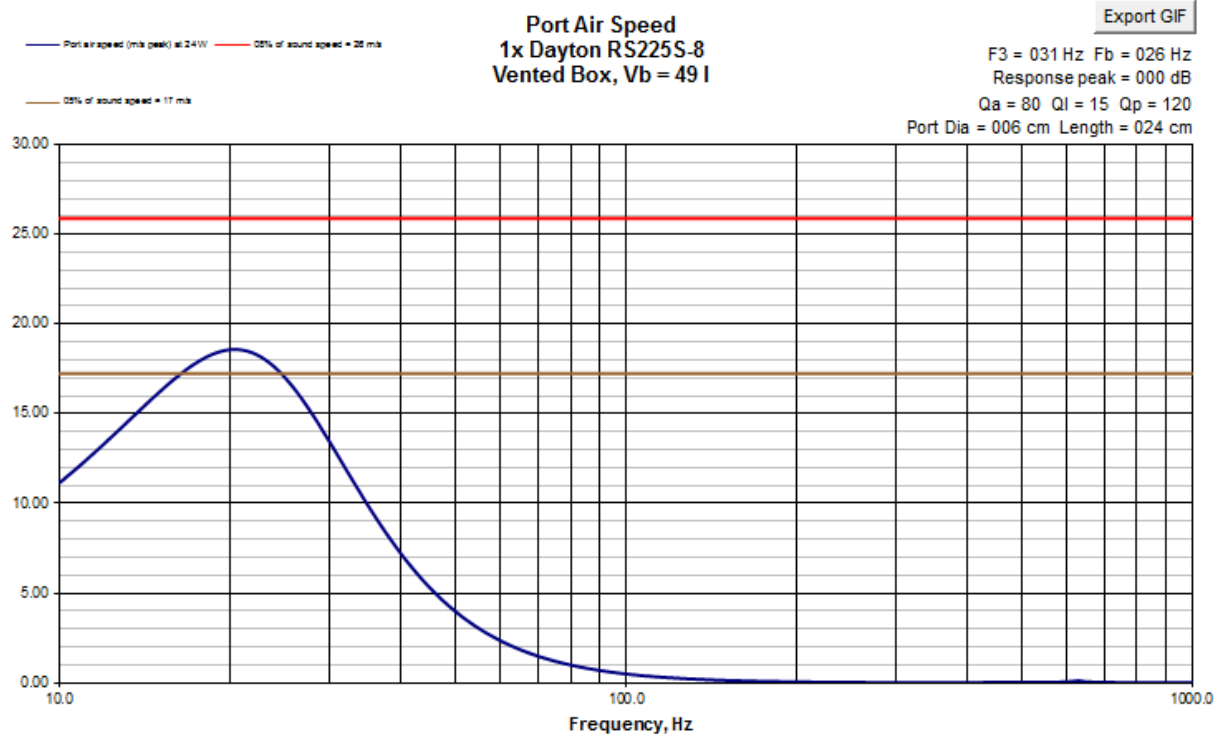


Transmission Line Loudspeaker Wizard

Schematic Diagram System Volume 50.584 Litres



S1	356.10
S2 Manual	356.10
S3	356.10
S4	30.88
L12 Con	57.00
L23 Con	83.00
L34 Par	0.01


Horn length is 163.59 cm

Schematic | Horn S1 - S4 | Save | Cancel

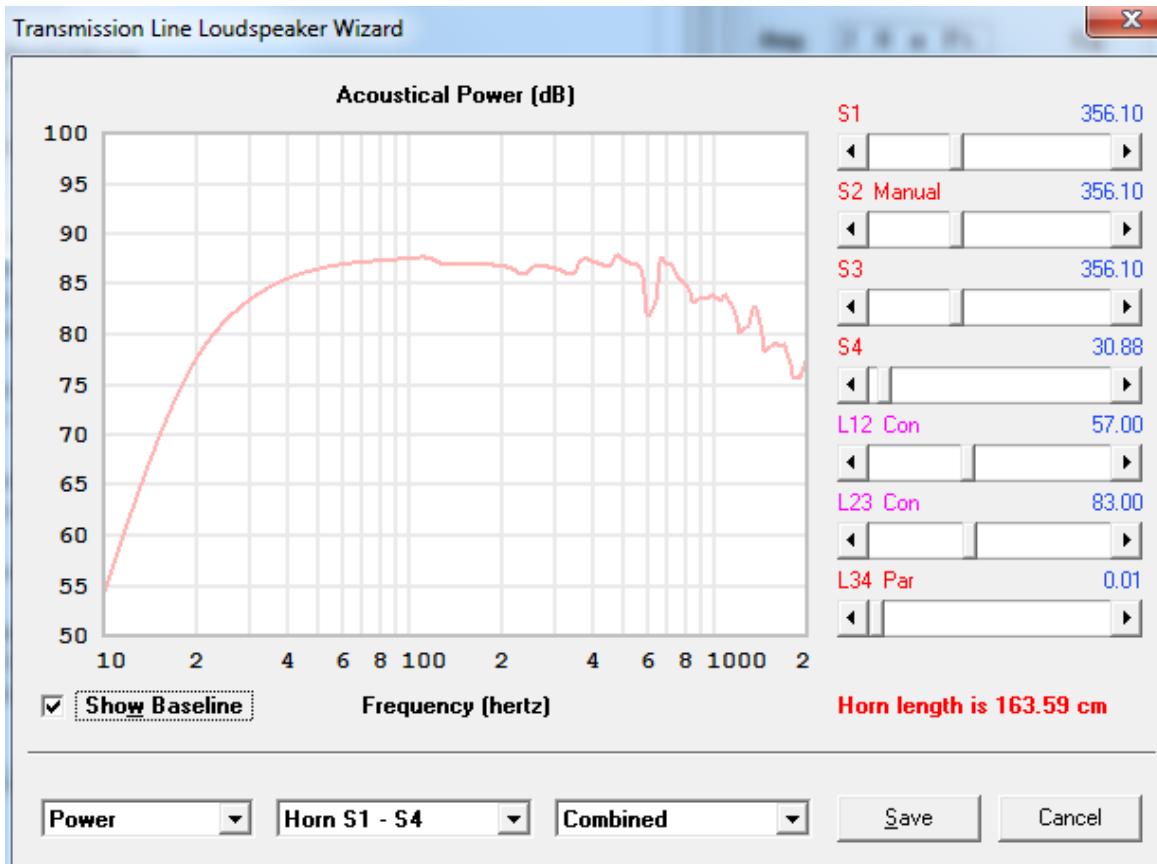

Results	
Response Model Parameters	
Sd, sq cm	84.9
Effective dia, cm	10.40
Driver Qts	0.46
Driver Fs	63.8
Listening distance, M	1
Baffle Specifications	
Baffle type:	r
Flat- Rectangle = R, Circle = C, U frame = U, H frame = H	
Dia of equivalent circular, cm	40.6713
Baffle Dimensions	
Flat Baffle Width (x) or Dia., or Sepaeation for H or U, cm.	21
Baffle height (y), cm	100
Driver Y position, cm	80
Drive X position, cm	10.5
Off axis angle, degrees	60
Max recommended Midrange baffle width or diameter:	
cm	20.79
in	8.19
Max SPL Input (Circular baffle)	
Xmax, mm	4
High Pass Crossover Fc	200
Equivalent Circular baffle	
Dipole Peak	847
Monopole = Dipole	282
First Dipole Null	1694
Max SPL at Fc, dB (2Pi)	108.0
Volume-Separation Product	690.599
Baffle Diffraction or Dipole Simulation	

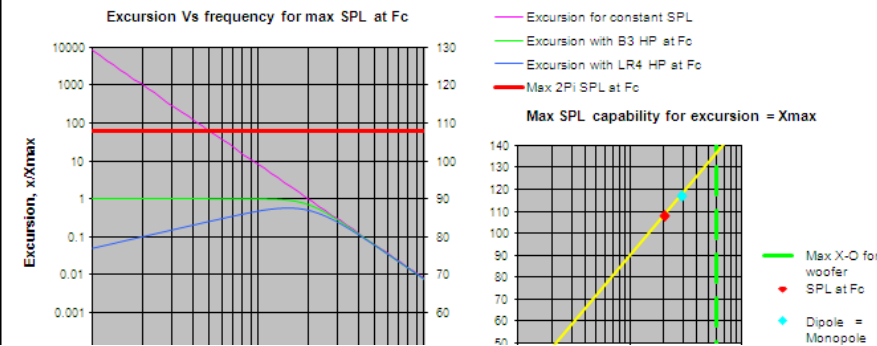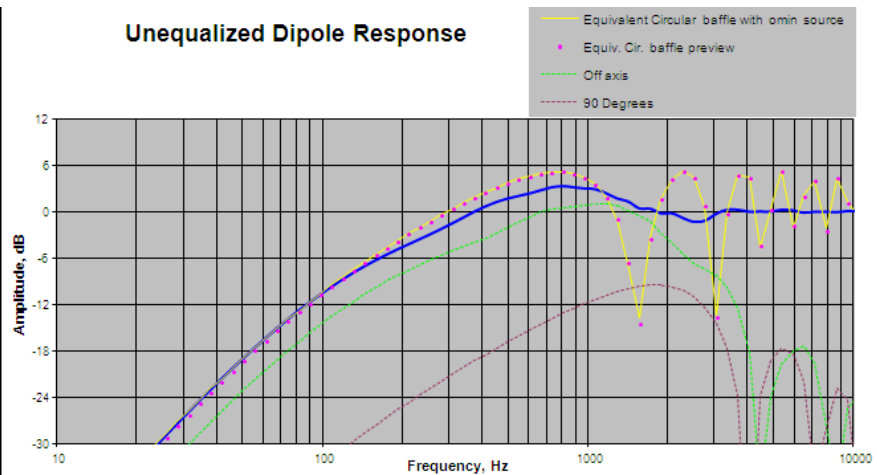

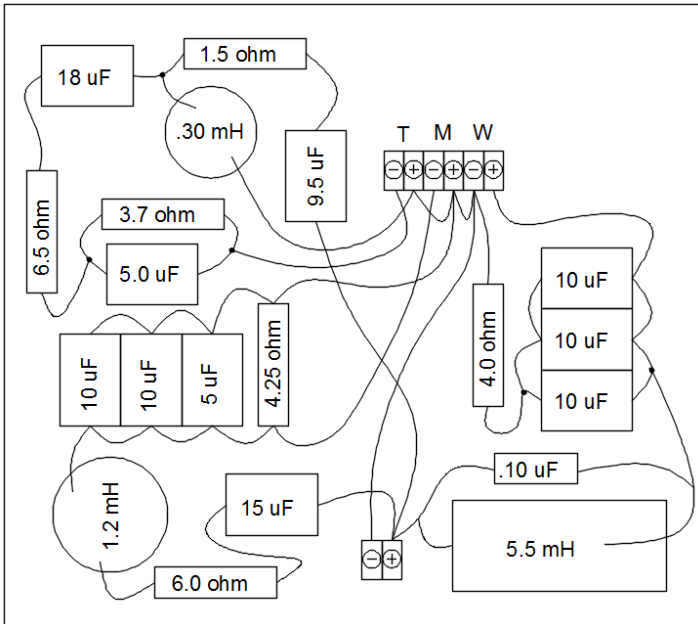

Baffle is 1.5 inches thick

